Application Note #3

Using Ray Allen RS 2 Rocker switch with no other switches

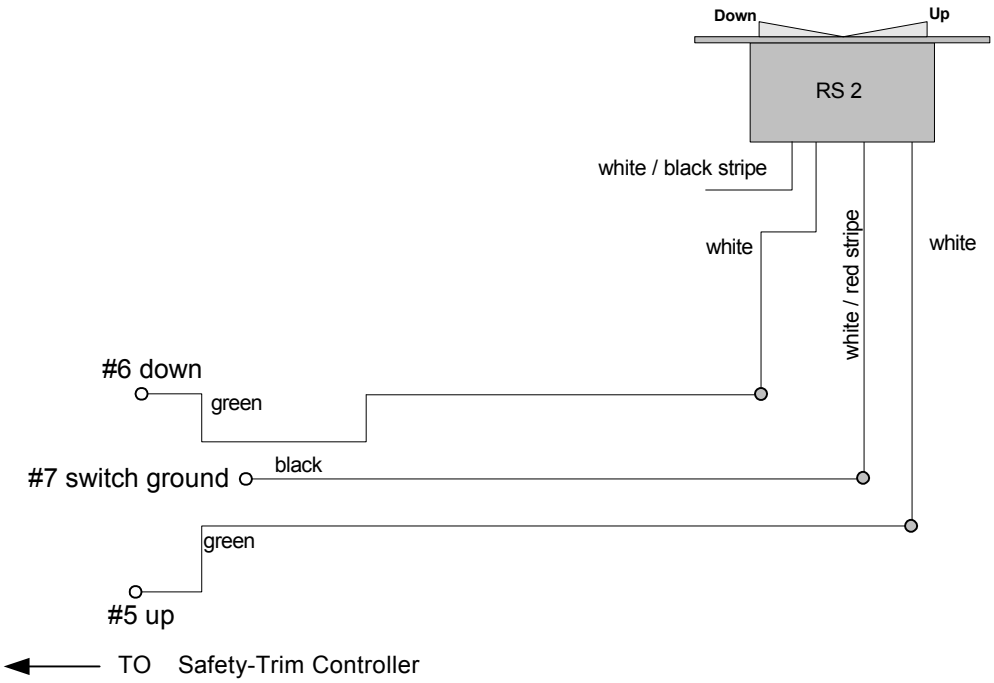

Note: RAY ALLEN Rocker Switch RS2 is of a custom design, in the neutral position the white wires are shorted together

Note: Aileron or Rudder trim switches may be wired in the same manner.